

# SPH3U UNIVERSITY PHYSICS

ELECTRICITY & MAGNETISM

Circuit Analysis  
(P.531-535)

---

---

---

---

---

---

---

---

## Analyzing Circuits

Before we can analyze a simple series or parallel electric circuit containing resistances we need to answer two basic questions:

1. What happens when we add resistances in series? in parallel?

October 8, 2012      3U4 - Circuit Analysis      1

---

---

---

---

---

---

---

---

## Analyzing Circuits

Before we can analyze a simple series or parallel electric circuit containing resistances we need to answer two basic questions:

2. Can we reduce multiple resistances to a single resistance? And if so, what is the equivalent resistance?

October 8, 2012      3U4 - Circuit Analysis      2

---

---

---

---

---

---

---

---

**Resistance in Series**

Consider an electric circuit with three resistors connected in series. Kirchhoff's laws and Ohm's law can be used to reduce the three resistors to a single resistor with an equivalent value of  $R_S$ .

$\therefore V_0 = V_1 + V_2 + V_3$   
 $\therefore I_0 R_S = I_1 R_1 + I_2 R_2 + I_3 R_3$   
 $\therefore I_0 = I_1 = I_2 = I_3$   
 $\therefore I_0 R_S = I_0 R_1 + I_0 R_2 + I_0 R_3$   
 or  **$R_S = R_1 + R_2 + R_3$**

October 8, 2012      3U4 - Circuit Analysis      3

---

---

---

---

---

---

---

---

**Resistance in Series**

**PRACTICE**

1. What is the equivalent resistor in a series circuit containing a 16  $\Omega$  light bulb, a 27  $\Omega$  heater, and a 12  $\Omega$  motor?

**$R_S = 55 \Omega$**

October 8, 2012      3U4 - Circuit Analysis      4

---

---

---

---

---

---

---

---

**Resistance in Series**

**PRACTICE**

2. Two identical unknown bulbs are connected in series with a 48  $\Omega$  and a 64  $\Omega$  heater to produce an equivalent resistance of 150  $\Omega$ . What is the resistance of each bulb?

**$R_1 = R_2 = 19 \Omega$**

October 8, 2012      3U4 - Circuit Analysis      5

---

---

---

---

---


---

---

---
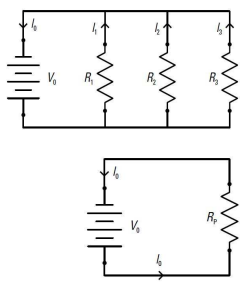
### Resistance in Parallel

We can use the same approach to find the equivalent resistance  $R_p$  of three resistors connected in parallel.



$\therefore I_0 = I_1 + I_2 + I_3$   
 $\therefore V_0/R_p = V_0/R_1 + V_0/R_2 + V_0/R_3$   
 $\therefore V_0 = V_1 = V_2 = V_3$   
 $\therefore V_0/R_p = V_0/R_1 + V_0/R_2 + V_0/R_3$   
 or  **$1/R_p = 1/R_1 + 1/R_2 + 1/R_3$**

October 8, 2012      3U4 - Circuit Analysis      6

---

---

---

---

---

---

---

---

### Resistance in Parallel

**PRACTICE**

3. Find the equivalent resistor when a 4  $\Omega$  bulb and a 8  $\Omega$  bulb are connected in parallel.

$R_p = 2.7 \Omega$

October 8, 2012      3U4 - Circuit Analysis      7

---

---

---

---

---

---

---

---

### Resistance in Parallel

**PRACTICE**

4. An unknown resistor is connected in parallel with a 30  $\Omega$  and a 40  $\Omega$  resistor to produce an equivalent resistance of 15  $\Omega$ . What is the resistance of the unknown resistor?

$R_3 = 120 \Omega$

October 8, 2012      3U4 - Circuit Analysis      8

---

---

---

---

---

---

---

---



### Equivalent Resistance in Mixed Circuits

**PRACTICE**

6. Calculate the equivalent resistance ( $R_{total}$ ) for the circuit shown.

$R_{parallel} = 15 \Omega$

$R_{total} = R_{series} = 45 \Omega$

$$\frac{1}{R_{parallel}} = \frac{1}{75} + \frac{1}{50} + \frac{1}{30}$$

$$R_{series} = 12 + 15 + 18$$

October 8, 2012      3U4 - Circuit Analysis      12

---

---

---

---

---

---

---

---

---

---

### Analyzing Circuits

*With what you've learned about electricity you should now be able to do a complete analysis of any simple series, parallel or mixed electric circuit containing resistances. However, because so many different electric circuits are possible, there is no standard approach to analyzing a circuit. The steps to take in each case will depend upon the information you have about the circuit, and what you want to find out.*

October 8, 2012      3U4 - Circuit Analysis      13

---

---

---

---

---

---

---

---

---

---

### Analyzing Circuits

**HINTS!**

- In most cases you can use KVL and KCL to find the values of two of  $V$ ,  $I$ , or  $R$ . You can then use  $V=IR$  to calculate the missing value.
- In some cases you must first reduce the circuit to a single equivalent resistance to find  $I_{SOURCE}$ .

October 8, 2012      3U4 - Circuit Analysis      14

---

---

---

---

---

---

---

---

---

---

**Analyzing Mixed Circuits**

**PRACTICE**

6. Find the missing values for the circuit given.

$I_1 = 6.0 \text{ A}$   
 $V_2 = 20.0 \text{ V}$   
 $I_4 = 1.0 \text{ A}$   
 $V_4 = 16.0 \text{ V}$   
 $V_5 = 16.0 \text{ V}$

October 8, 2012      3U4 - Circuit Analysis      15

---

---

---

---

---

---

---

---

**Analyzing Mixed Circuits**

**PRACTICE**

7. Find  $V_1$ ,  $V_2$ ,  $V_3$ ,  $I_1$ ,  $I_2$ ,  $I_3$  and  $R_2$  for the circuit given.

$I_1 = 12 \text{ A}$   
 $V_1 = 96 \text{ V}$   
 $V_3 = 24 \text{ V}$   
 $I_3 = 8.0 \text{ A}$   
 $V_2 = 24 \text{ V}$   
 $I_2 = 4.0 \text{ A}$   
 $R_2 = 6.0 \Omega$

October 8, 2012      3U4 - Circuit Analysis      16

---

---

---

---

---

---

---

---

**Analyzing Mixed Circuits**

**PRACTICE**

8. Complete each circuit given by finding the unknown quantities indicated.

(a)  $I_0$ ,  $I_1$ ,  $I_2$ ,  $V_1$ ,  $V_2$

(a)  $I_0 = I_1 = I_2 = 0.5 \text{ A}$  (KCL)  
 $V_1 = 2.5 \text{ V}$   
 $V_3 = 3.5 \text{ V}$

October 8, 2012      3U4 - Circuit Analysis      17

---

---

---

---

---

---

---

---

**Analyzing Mixed Circuits**

**PRACTICE**

8. Complete each circuit given by finding the unknown quantities indicated.

(b)  $V_1, V_2, I_0, I_1, I_2$

(b)  $V_1 = V_2 = 6.0 \text{ V}$  (KVL)  
 $I_1 = 1 \text{ A}$   
 $I_2 = 2 \text{ A}$   
 $I_0 = 3 \text{ A}$

October 8, 2012      3U4 - Circuit Analysis      18

---

---

---

---

---

---

---

---

**Activity: Analyzing Circuits (Inv.11.8.1/P.536)**

**INSTRUCTIONS**

A. Follow procedure steps 1-16.

B. For parts A and B use the following:

- one source ( $V_{\text{source}} = 10 \text{ V}$ )
- two resistors ( $R_1 = 5 \Omega$  &  $R_2 = 20 \Omega$ )

C. For part C use the following:

- one source ( $V_{\text{source}} = 10 \text{ V}$ )
- four resistors ( $R_1 = 10 \Omega, R_2 = 5 \Omega, R_3 = 15 \Omega, \text{ \& } R_4 = 20 \Omega$ )
- mixed circuit diagram (Q.1(c)/P.535)

**NOTE!**  
 You will be using an electronic circuit construction kit. Do a Google search for **phet dc kit**.

October 8, 2012      3U4 - Circuit Analysis      19

---

---

---

---

---

---

---

---

**Activity: Analyzing Circuits (Inv.11.8.1/P.536)**

**QUESTIONS**

P.537 Q.(b)-(h)

P.535 Q.2-4/P.535      be neat and be sure to show your work!

October 8, 2012      3U4 - Circuit Analysis      20

---

---

---

---

---

---

---

---