

SPH3U


UNIVERSITY PHYSICS

ELECTRICITY & MAGNETISM

- ✦ Electrical Resistance
- (P.523-526)

Electrical Resistance

*When charges pass through a material or device, they experience an opposition or **electrical resistance (R)** to their flow, resulting in a loss of electric potential energy. Resistance is measured in ohms (Ω). All substances resist the flow of charges to some extent.*




ELECTRICAL RESISTANCE (R)

- ✦ degree to which a substance resists the flow of electric current through it
- ✦ SI unit is ohm (Ω)

September 22, 2012 3U4 - Electrical Resistance 1

Electrical Resistance

Resistors are electrical devices that have a specific resistance. There are many different types of resistors. For example, lightweight carbon resistors are used in electronics; heavier ceramic resistors are used in larger circuits. Dimmer switches and the volume controls on a stereo are examples of variable resistors – resistors that allow you can change their resistance.



RESISTOR

- ✦ any material that can slow current flow
- ✦ circuit symbol is $\text{---}\text{/\!/\!/\text{---}}$

September 22, 2012 3U4 - Electrical Resistance 2

Electrical Resistance

To measure the amount of resistance that a quantity of moving charge encounters, we compare the electric potential difference the charge experiences as it passes through a load with the amount of electric current.

September 22, 2012 3U4 - Electrical Resistance 3

Electrical Resistance

By varying the potential difference of the source and making simultaneous measurements of current (I) and potential difference (V), the following graph of V vs I can be obtained. From the graph we see that the ratio V/I (i.e. the resistance) is a constant.

NOTE!
German physicist Georg Ohm used this ratio to formulate Ohm's Law. **Ohm's Law** states that, as long as the temperature remains constant, $V = IR$.

slope = $\frac{\text{rise}}{\text{run}}$
 slope = $\frac{\text{voltage (V)}}{\text{current (I)}}$
 slope = resistance (R)

September 22, 2012 3U4 - Electrical Resistance 4

Electrical Resistance

RECALL!
A material that obeys Ohm's Law is said to be "ohmic." Thus, a straight line on a $V-I$ graph indicates an "ohmic" material whereas a curved line indicates a "non-ohmic" material.

slope = $\frac{\text{rise}}{\text{run}}$
 slope = $\frac{\text{voltage (V)}}{\text{current (I)}}$
 slope = resistance (R)

September 22, 2012 3U4 - Electrical Resistance 5

Ohm's Law

OHM'S LAW
 ✦ as long as the temperature stays constant (i.e. $V \propto I$)

$V = IR$

$V=IR \quad I=V/R \quad R=V/I$

where V is the potential difference (V)
 I is the current (A)
 R is the resistance (Ω)

September 22, 2012 3U4 - Electrical Resistance 6

Ohm's Law

PRACTICE

1. What is the potential difference across a toaster of resistance of 13.8Ω when the current through it is 8.7 A ?

$V = 120 \text{ V}$

September 22, 2012 3U4 - Electrical Resistance 7


Ohm's Law

PRACTICE

2. Calculate the resistance of a load with a voltage of 25 V and a current of 410 mA .

$R = 61 \Omega$

September 22, 2012 3U4 - Electrical Resistance 8


 Ohm's Law

PRACTICE

3. In a circuit where voltage is kept constant, state what happens to the current if the resistance is doubled? quadrupled? halved? (Hint: since $I = V/R$ then $I \propto 1/R$)

$I \times \frac{1}{2}$
 $I \times \frac{1}{4}$
 $I \times 2$

September 22, 2012 3U4 - Electrical Resistance 9


 Ohm's Law

PRACTICE

4. Find the missing values in the table below. Take care with units.

Current	Voltage (V)	Resistance (Ω)
25 mA	12	480
1.2 A	612	510
375 μ A	0.250	667
3.6 A	120	33
667 mA	1.5	1500

September 22, 2012 3U4 - Electrical Resistance 10

 **✓ Check Your Learning**

TEXTBOOK
 P.526 Q.2-6,9,12

September 22, 2012 3U4 - Electrical Resistance 11
